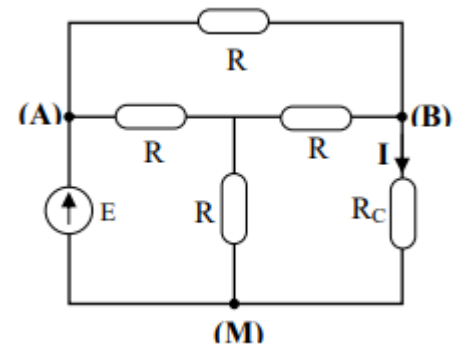
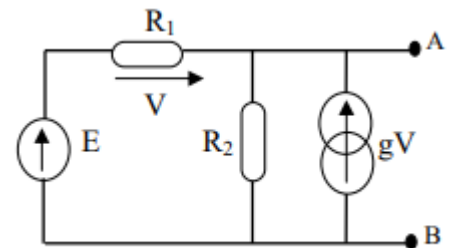


**Module:** Electricity**Tutorial Worksheet No. 6:****Duration:** 3 weeks**Exercises to do in class:** 1,2,4,5,7,10**Assignment to submit:** 3,6,8,9**Exercise 1: (Week 1)**Given:  $E = 1^V$ ,  $R = 2^{k\Omega}$ ,  $R_C = 1^{k\Omega}$ 

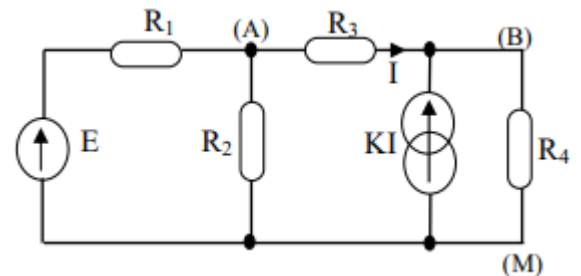
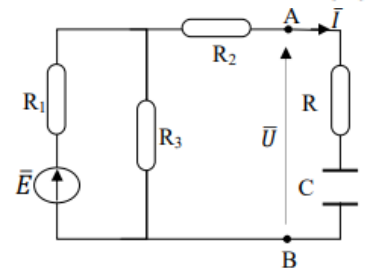
- Determine the elements ( $E_{th}$ ,  $R_{th}$ ) of the Thevenin generator, as seen from terminals B and M by resistance  $R_C$ .
- Determine the short-circuit current  $I_{SC}$  of branch BM. ( $R_C=0$ )
- Verify the equivalence of generators ( $E_{th}$ ,  $R_{th}$ ) and ( $I_{SC}$ ,  $R_{th}$ ). Deduce the current  $I$ .

**Exercise 2: (Week 1)**


- In the following circuit, what type of controlled source is it?
- Determine the equivalent Thevenin circuit ( $E_{th}$ ,  $R_{th}$ ) as seen between poles A and B.
- Express the current  $I_N$  of the equivalent Norton generator.
- Verify the Thevenin-Norton equivalence.

Given:  $E = 1V$ ;  $g = 5mA/V$ ;  $R_1 = R_2 = 2k\Omega$ **Exercise 3:**Given:  $E = 1V$ ;  $K = 50$ ;  $R_1 = R_2 = 2k\Omega$ ;  $R_3 = 1k\Omega$ ;  $R_4 = 40\Omega$ Calculate the current  $I_4$  in branch BM of the circuit using:

- The nodal analysis method
- The Thevenin-Norton theorem

**Exercise 4: (Week 2)**Given:  $\underline{E} = 50^V \angle 0^\circ$ ;  $\omega = 5000rad/s$ ;  $R_1 = 200\Omega$ ;  $R_2 = 210\Omega$ ;  $R_3 = R = 50\Omega$ ;  $C = 2\mu F$ Calculate the elements ( $I_N$ ,  $R_N$ ) of the Norton generator as seen by dipole AB.Deduce the value of current  $I$  in this dipole.**Exercise 5: (Week 2)**Given:  $R_1 = 1k\Omega$ ;  $R = 2k\Omega$ ;  $R_2 = 100\Omega$ ;  $R_L = 5k\Omega$ ;  $k = 0.5 \times 10^3 \Omega$ ;  $e = 15V$ ;  $r = 50\Omega$ 

- Write the nodal equations in ordered literal form. Deduce the values of voltages  $V_1$  and  $V_2$ .
- Determine  $E_T$  and resistance  $R_T$  of the Thevenin generator equivalent to the circuit as seen by load  $R_L$ .
- Give the expression for the current  $I_N$  of the Norton generator equivalent to the circuit as seen by load  $R_L$ .
- Use the Thevenin-Norton equivalence to verify the obtained results.

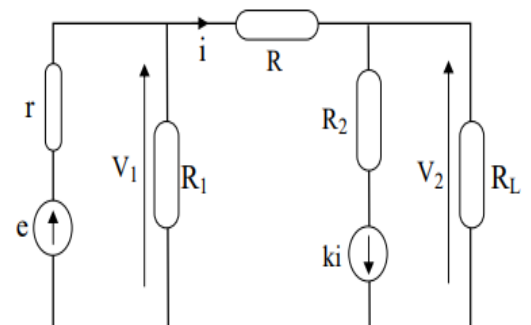

**Exercise 6:**

Given:  $E = 10\angle 0^\circ \text{ V}$ ; Circuit contains impedances:  $5\Omega$ ,  $j5\Omega$ ,  $3\Omega$ ,  $j4\Omega$

Calculate the elements ( $E_{th}$ ,  $Z_{th}$ ) and ( $I_N$ ,  $Z_N$ ) of the Thevenin and Norton generators respectively, as seen by dipole AB. Verify the Thevenin-Norton equivalence.

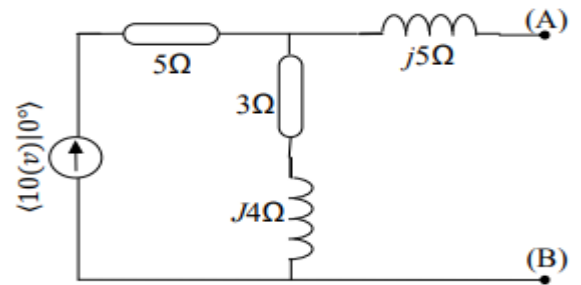
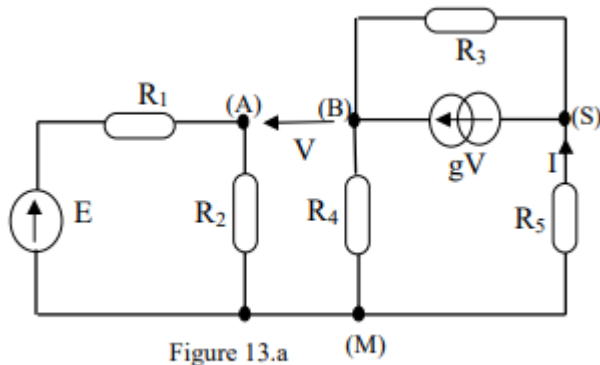
**Exercise 7: (Week 3)**

Figure 13.a

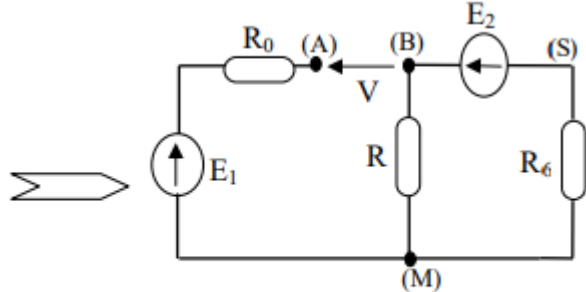


Figure 13.b

Given:  $E = 1\text{ V}$ ;  $g = 5\text{ mA/V}$ ;  $R_1 = R_2 = 2\text{ k}\Omega$ ;  $R_3 = 2\text{ k}\Omega$ ;  $R_4 = 200\Omega$ ;  $R_5 = 4.8\text{ k}\Omega$

The circuit in figure 13.a transforms into an equivalent schematic given by figure 13.b:

a) Determine the elements  $E_1$ ,  $E_2$ ,  $R_0$ ,  $R$ , and  $R_6$  of the circuit.

b) Determine the current  $I$  in branch SM using:

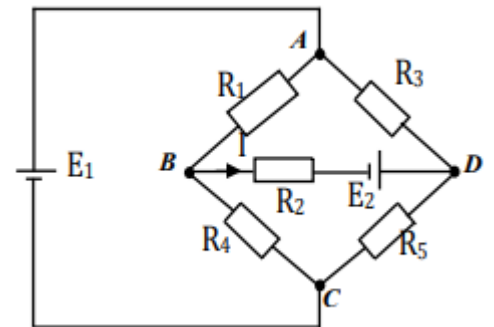
- The mesh analysis method
- The Thevenin-Norton theorem

**Exercise 8:**

Given:  $E_1 = 10\text{ V}$ ;  $E_2 = 5\text{ V}$ ;  $R_1 = 6\Omega$ ;  $R_2 = 50\Omega$ ;  $R_3 = 100\Omega$ ;  $R_4 = 14\Omega$ ;  $R_5 = 46\Omega$


Calculate current  $I$  by applying:

- The Thevenin theorem
- The superposition theorem

**Exercise 9:**

Given:  $R_1 = 1\text{ k}\Omega$ ;  $R_3 = 2\text{ k}\Omega$ ;  $R_2 = 100\Omega$ ;  $R_4 = 5\text{ k}\Omega$ ;  $E = 15\text{ V}$ ;  $J = 50\text{ mA}$


By applying the superposition theorem, calculate the current  $I$  in branch AM.

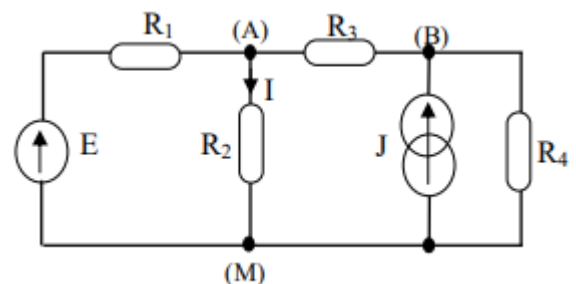**Exercise 10: (Week 3)**

Given:  $R_1 = R_2 = 1\text{ k}\Omega$ ;  $R_3 = 2\text{ k}\Omega$ ;  $R = 250\Omega$ ;  $E = 10\text{ V}$ ;  $J = 100\text{ mA}$

a) Using Kennelly's theorem, transform the delta connection of  $R_1$ ,  $R_2$ , and  $R_3$  into a wye (star) connection.









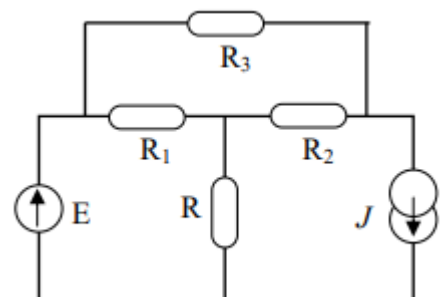
b) Calculate the current through resistance  $R$  using the principle of superposition.







### Exercise 11:

Given the 13 circuits below to analyze. Calculate the current  $i$  for each circuit using:

1. Thevenin method
2. Norton method

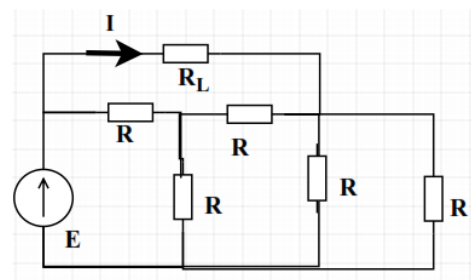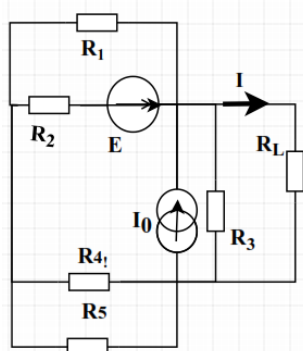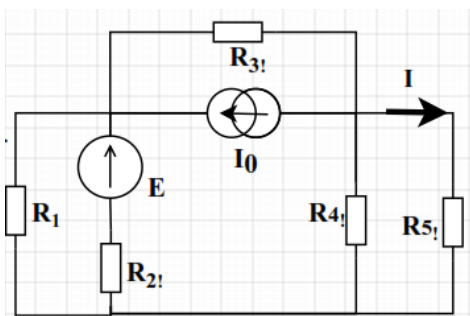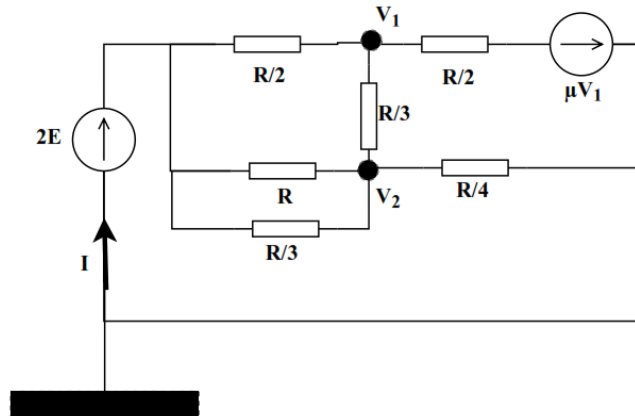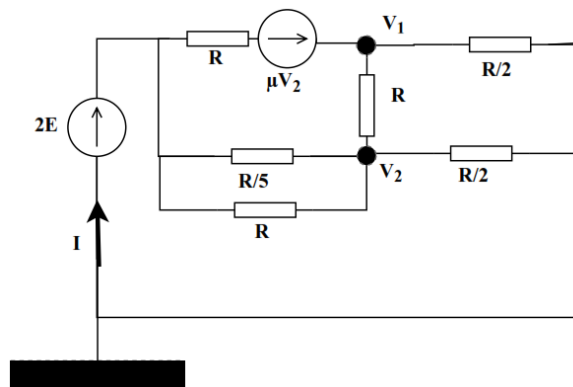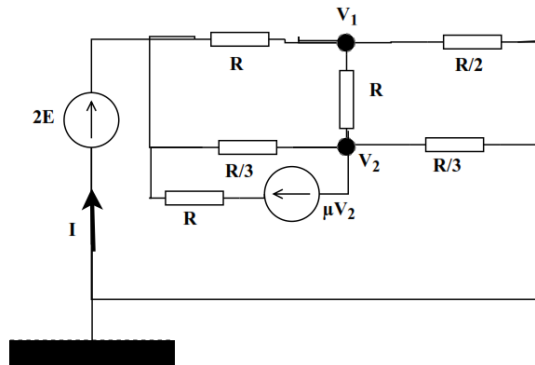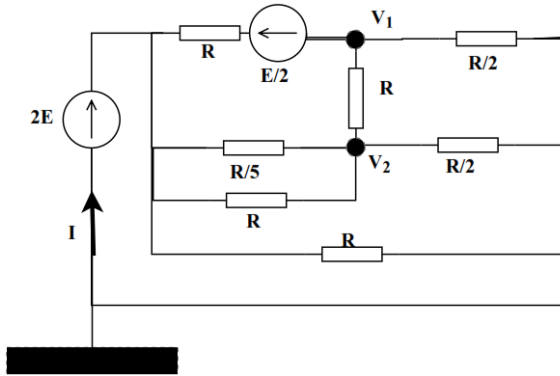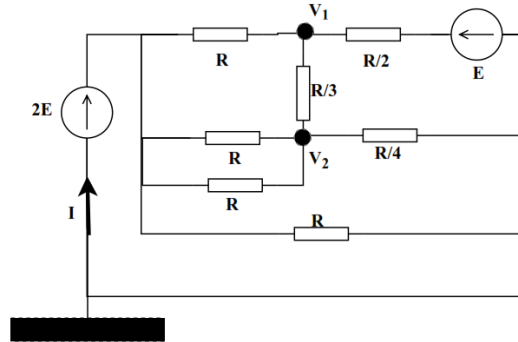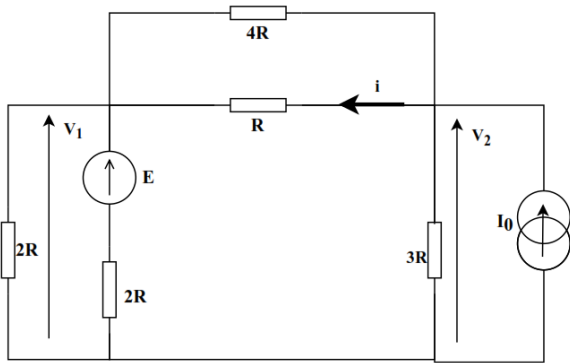

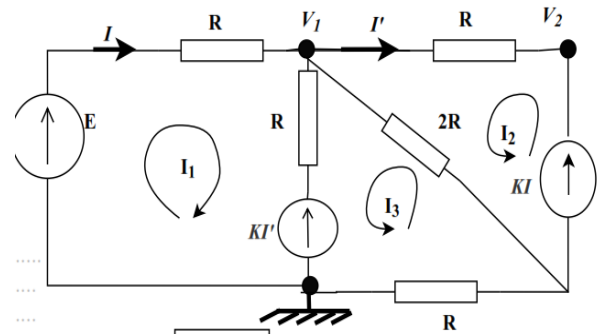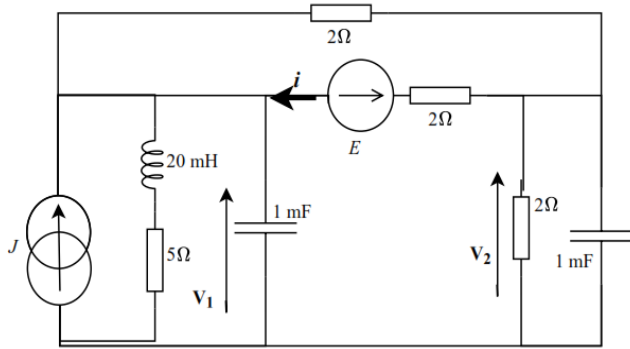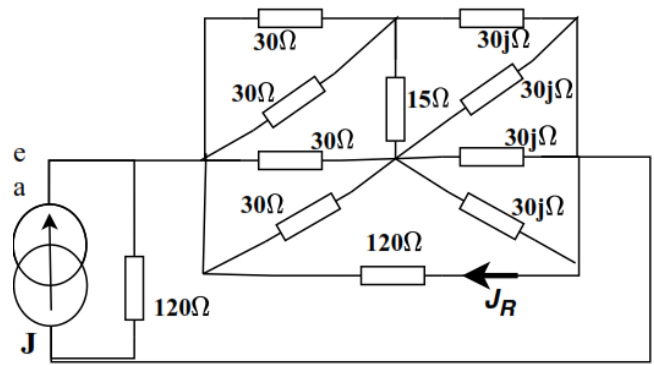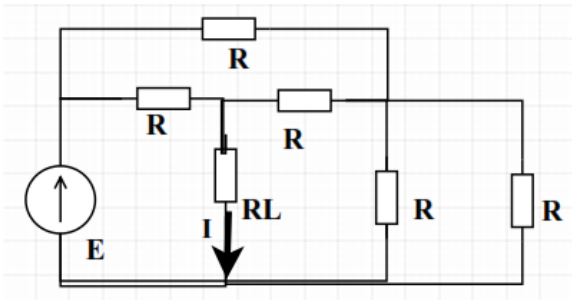


### Exercise 12:

Find the current  $I$  using the following methods:

- Thevenin method
- Norton method

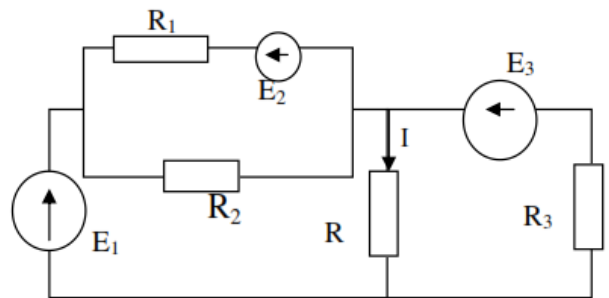
#### Circuit 1

$E_1 = E_2 = 10V$   
 $R_1 = R_3 = 10\text{ k}\Omega$   
 $R = R_2 = 5\text{ k}\Omega$   
 $E_3 = 5V$



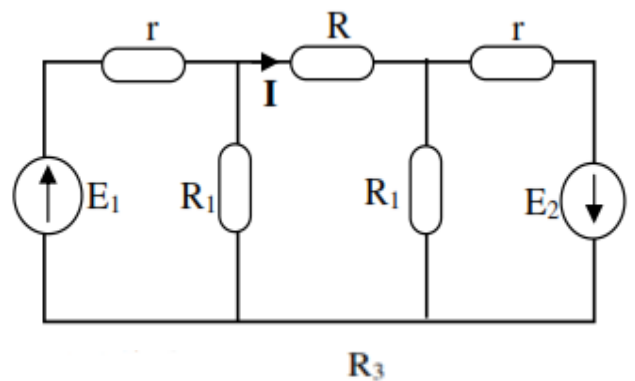
#### Circuit 2

$E_1 = 1\text{ V}$ ,  
 $E_2 = 2V$ ,  
 $r = 500\Omega$ ,  
 $R = 1\text{ k}\Omega$ ,  
 $R_1 = 1,5\text{ K}\Omega$  ;


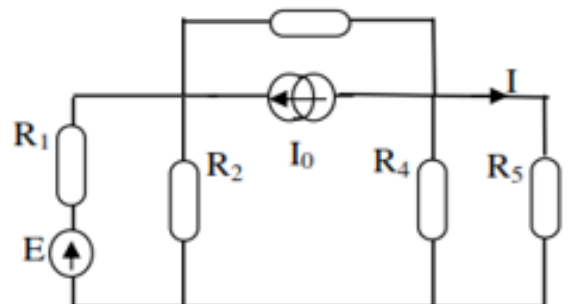
#### Circuit 3

$E = 10V$  ,  
 $I_0 = 0.1\text{ A}$ ,  
 $R_1 = 10\Omega$ ,  
 $R_2 = 15\Omega$ ,  
 $R_3 = 8\Omega$ ,  
 $R_4 = 14\Omega$ ,  
 $R_5 = 5\Omega$




### Circuit 4

$$E = 12 \text{ [V]}$$

$$R_i = R$$

$$I_{R3} = ?$$

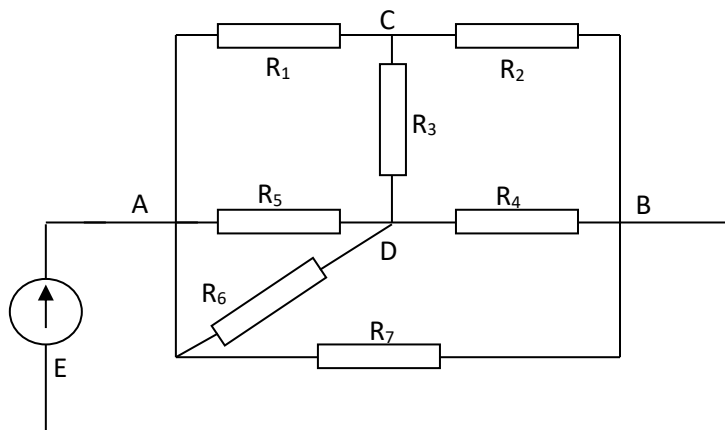

### Circuit 5

$$R_1 = 0,2 \text{ k}\Omega$$

$$E = 0,1 \text{ mV}$$


$$R_2 = R_6 = 1 \text{ k}\Omega$$

$$J = 10 \text{ mA}$$

$$R_3 = 2 \text{ k}\Omega$$

$$R_4 = 0,5 \text{ k}\Omega$$


$$R_5 = 3 \text{ k}\Omega$$

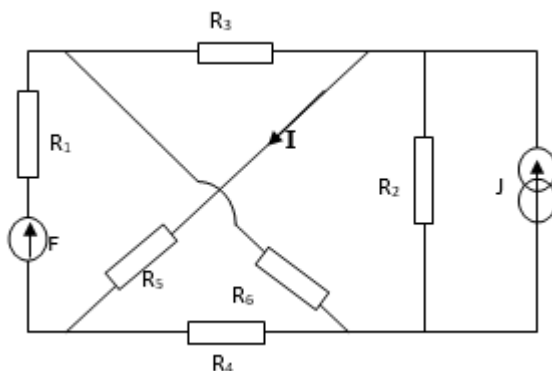
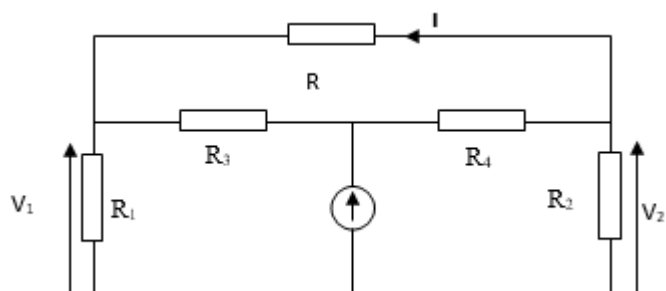
### Circuit 6

$$R_1 = 1 \text{ k}\Omega, R_2 = 0,5 \text{ k}\Omega, R_3 = 0,33 \text{ k}\Omega, R_4 = 0,25 \text{ k}\Omega$$


$$R = 0,1 \text{ k}\Omega, e = 12,4 \text{ V}$$


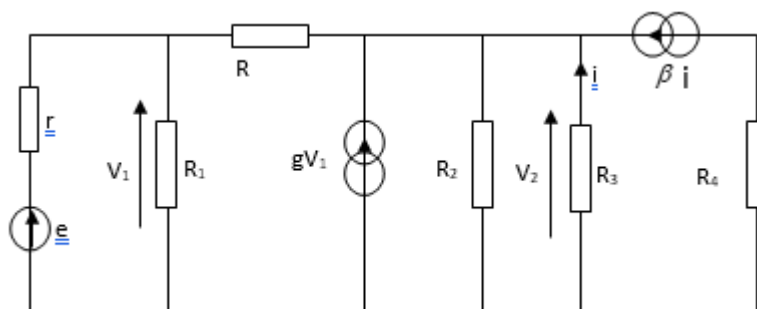
### Circuit 7

$$r = 10 \text{ }\Omega, R_1 = 2 \text{ k}\Omega, R_2 = R_3 = 5 \text{ k}\Omega,$$

$$R = 1/g = 1 \text{ k}\Omega, e = 1 \text{ V}, \beta = 50$$



### Circuit 8

