

**Module:** Electricity

**Tutorial Worksheet No. 5:**

**Duration:** 3 weeks (one method / week)

**Exercises to do in class:** 1 , 2

**Assignment to submit:** 3

**Exercise 1:**

**Part A**

Find the voltages  $V_1$  and  $V_2$  using the following methods:

- The mesh current method
- The nodal voltage method
- The superposition method

We have :

$$E_1 = 20\sqrt{2} \sin(\omega t) \text{ [V]}$$

$$E_2 = 10\sqrt{2} \sin(\omega t) \text{ [V]}$$

$$I_0 = 3\sqrt{2} \sin(\omega t) \text{ [A]}$$

$$R = 10 \text{ } [\Omega]$$

**Part B**

Find the current  $I$  using the following methods:




- The mesh current method
- The nodal voltage method

**Exercise 2:**

Consider the circuit below, composed of two voltage sources with RMS values  $E$  and  $E/2$ , a voltage-controlled current source (VCCS) with voltage  $V$  (with a gain  $g = 20/R$ ), and 6 identical resistances of value  $R$ .

Find the voltage  $U$  using:







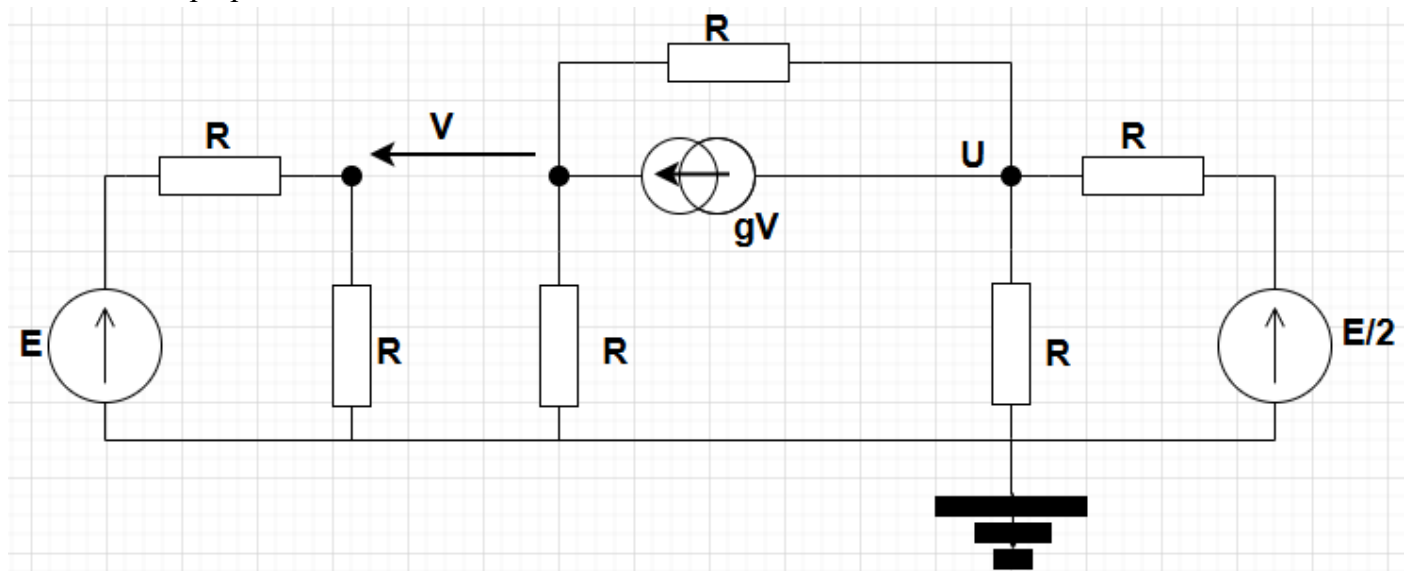
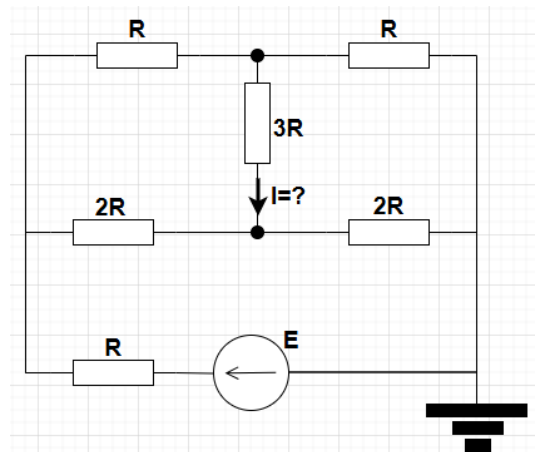
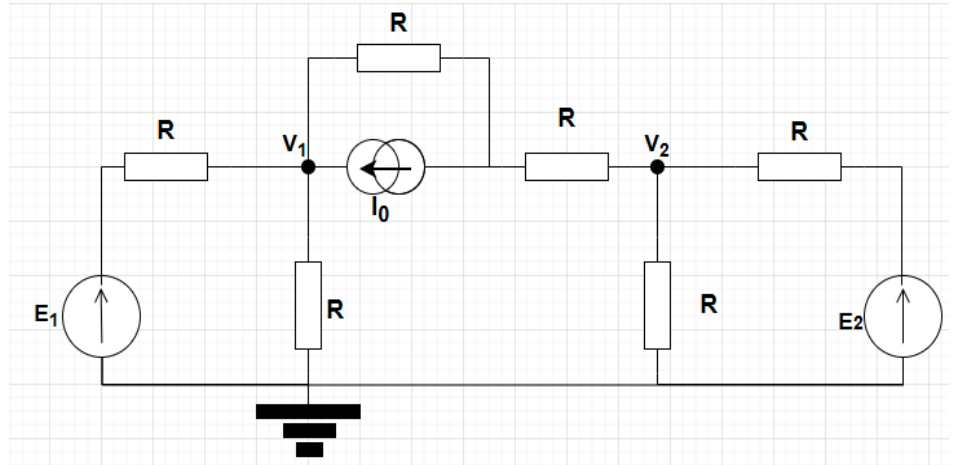
- The mesh current method
- The nodal voltage method
- The superposition method







### Exercise 3:

Given the 13 circuits below to analyze. Calculate the current  $i$  for each circuit using:

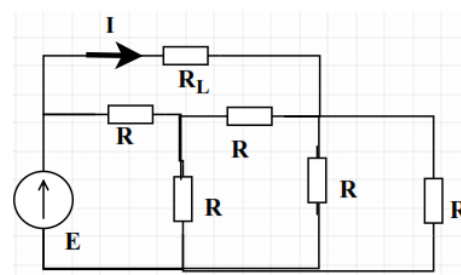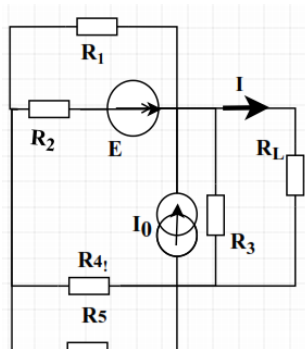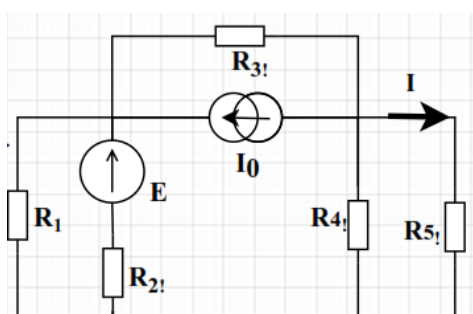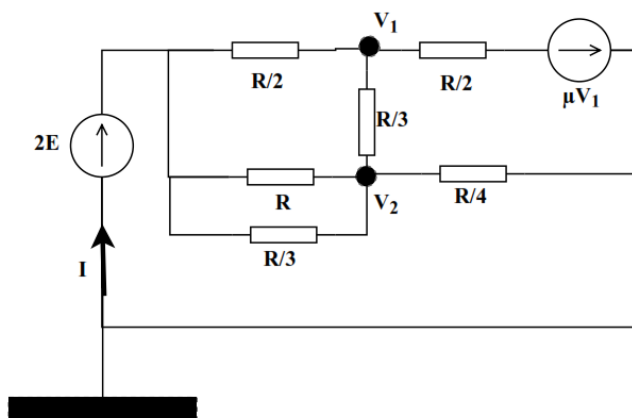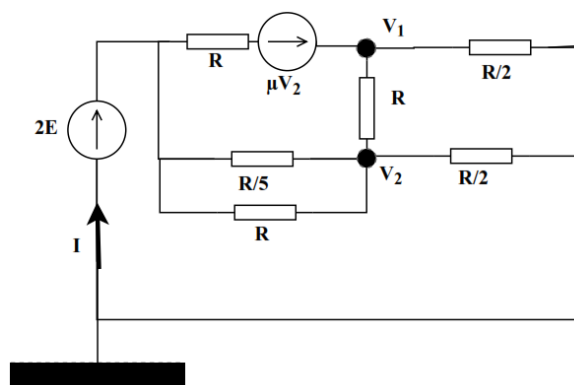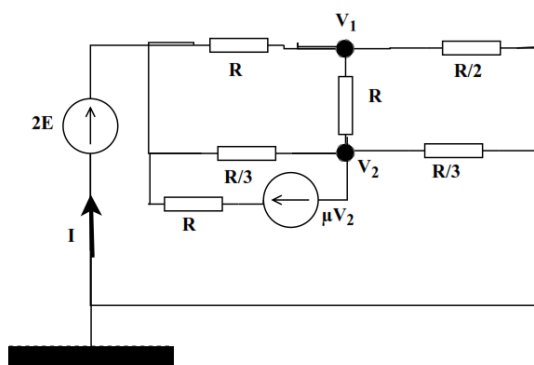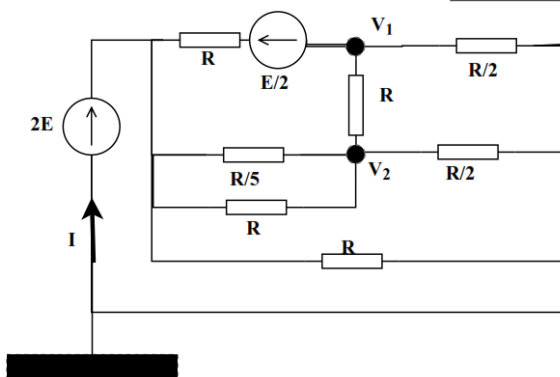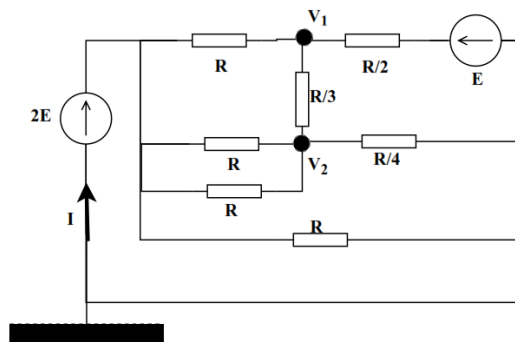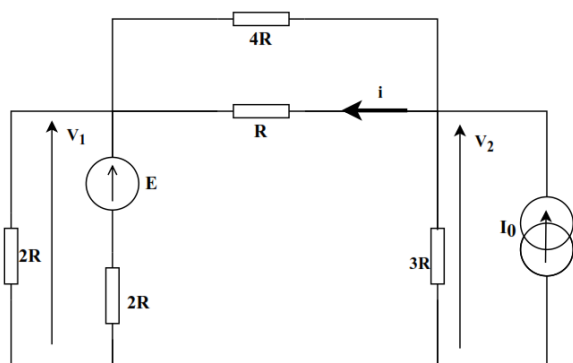1. The mesh current method
2. The nodal voltage method
3. The superposition method



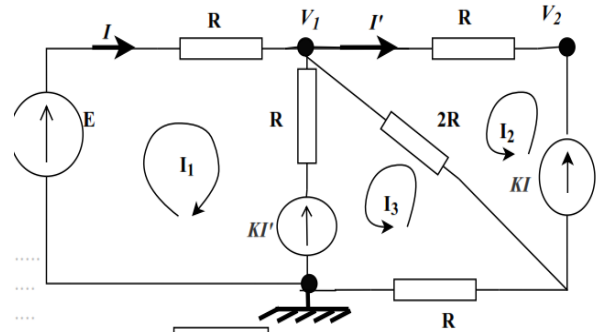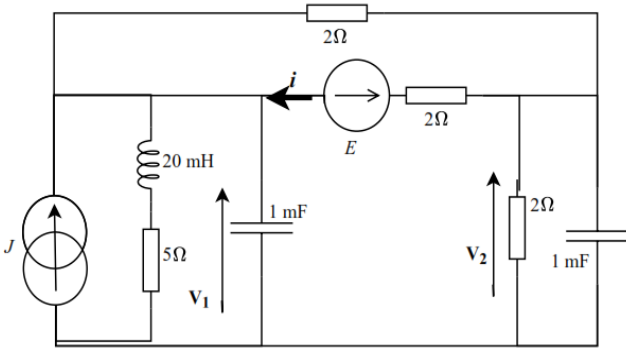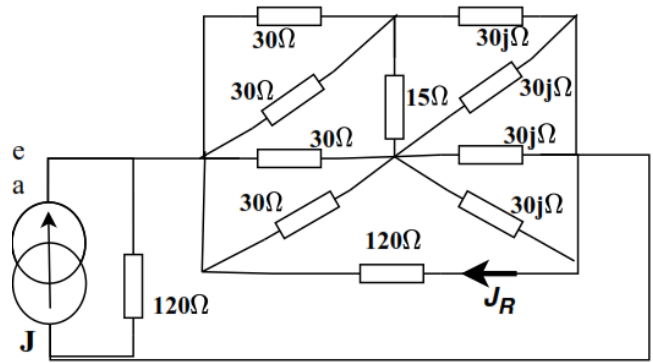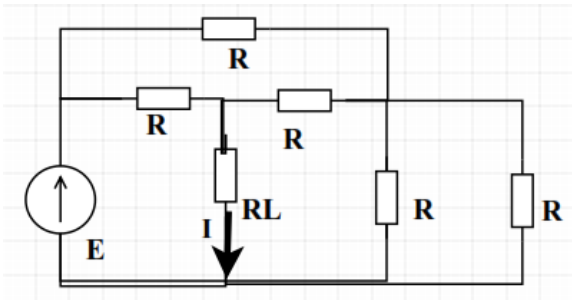


#### Exercise 4:

Find the current  $I$  using the following methods:

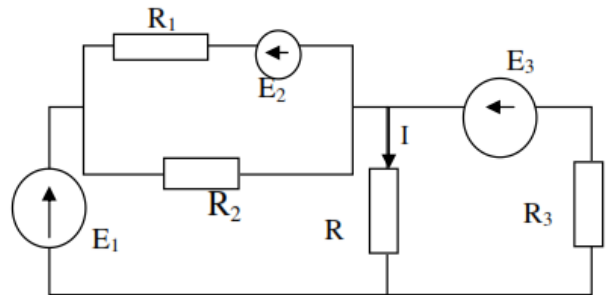
##### Circuit 1

$E_1 = E_2 = 10\text{V}$   
 $R_1 = R_3 = 10\text{ k}\Omega$   
 $R = R_2 = 5\text{ k}\Omega$   
 $E_3 = 5\text{V}$



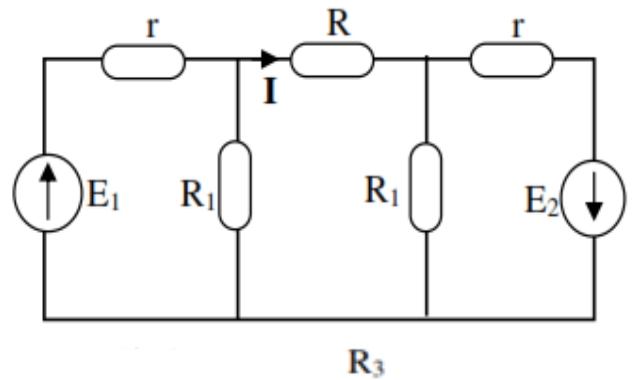
##### Circuit 2

$E_1 = 1\text{ V}$ ,  
 $E_2 = 2\text{V}$ ,  
 $r = 500\Omega$ ,  
 $R = 1\text{ k}\Omega$ ,  
 $R_1 = 1,5\text{ K}\Omega$  ;


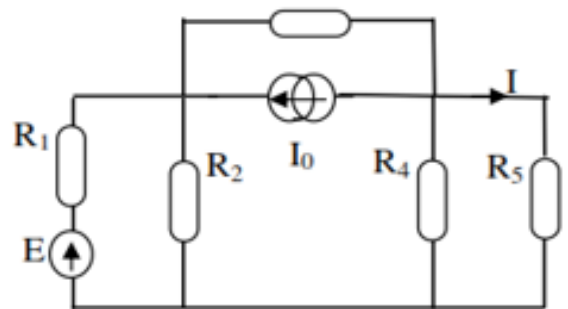
##### Circuit 3

$E = 10\text{V}$  ,  
 $I_0 = 0.1\text{ A}$ ,  
 $R_1 = 10\Omega$ ,  
 $R_2 = 15\Omega$ ,  
 $R_3 = 8\Omega$ ,  
 $R_4 = 14\Omega$ ,  
 $R_5 = 5\Omega$




### Circuit 4

$$E = 12 \text{ [V]}$$

$$R_i = R$$

$$I_{R3} = ?$$

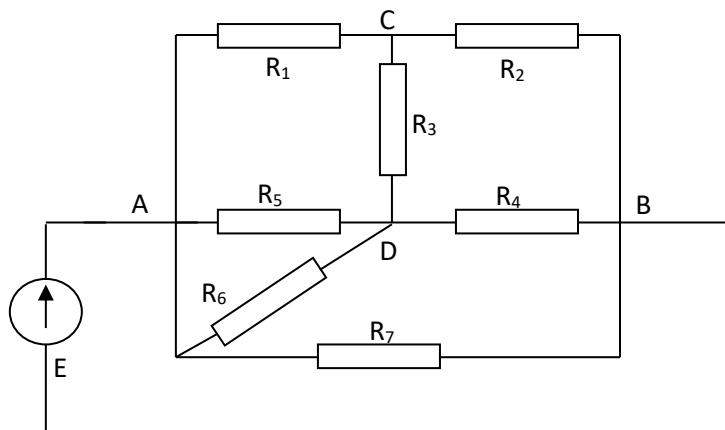

### Circuit 5

$$R_1 = 0,2 \text{ k}\Omega$$

$$E = 0,1 \text{ mV}$$


$$R_2 = R_6 = 1 \text{ k}\Omega$$

$$J = 10 \text{ mA}$$

$$R_3 = 2 \text{ k}\Omega$$

$$R_4 = 0,5 \text{ k}\Omega$$


$$R_5 = 3 \text{ k}\Omega$$

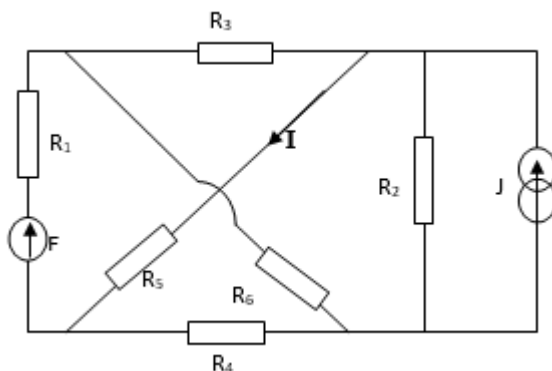
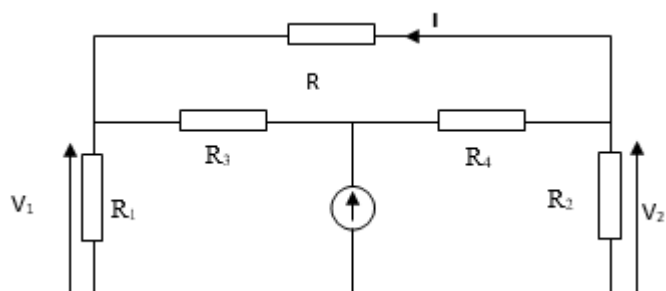
### Circuit 6

$$R_1 = 1 \text{ k}\Omega, R_2 = 0,5 \text{ k}\Omega, R_3 = 0,33 \text{ k}\Omega, R_4 = 0,25 \text{ k}\Omega$$


$$R = 0,1 \text{ k}\Omega, e = 12,4 \text{ V}$$


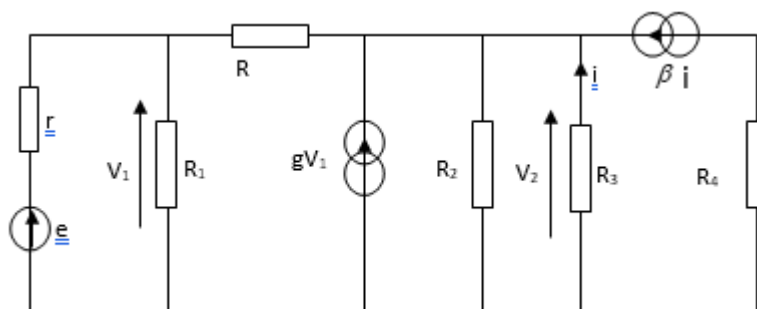
### Circuit 7

$$r = 10 \text{ }\Omega, R_1 = 2 \text{ k}\Omega, R_2 = R_3 = 5 \text{ k}\Omega,$$

$$R = 1/g = 1 \text{ k}\Omega, e = 1 \text{ V}, \beta = 50$$



### Circuit 8

